

**The Bottle Builder**  
A Compendium of Tube Amp Designs  
Volume 1

Johan Basse Bergqvist

---

**Table of Contents**

<b>Introduction</b> . . . . .	<b>15</b>
About the Designs . . . . .	17
Conventions used in this book . . . . .	18
The Hype . . . . .	18
The Real McCoy . . . . .	20
Choice of Components . . . . .	22
Good Practices . . . . .	24
Heater Wiring . . . . .	25
Ground loops . . . . .	25
Hazards . . . . .	25
Disclaimer . . . . .	26
<b>1. BLUBOTTLE – small amp, big sound</b> . . . . .	<b>27</b>
General circuit description (left channel referenced) . . . . .	27
The Tone Control . . . . .	28
The Phono Stage . . . . .	28
Coupling capacitors . . . . .	29
Indicator Tubes . . . . .	29
The Power Supply . . . . .	29
Building and Tuning . . . . .	30
Powering up for the first time . . . . .	32
Problems . . . . .	32
Maintenance . . . . .	32
Chassis mounting . . . . .	32
Bill of Materials . . . . .	33
<b>2. Octopus, the Octal lover’s 2 x 8W integrated amplifier with MS option</b> . . . . .	<b>47</b>
The tone control . . . . .	47
Volume and balance controls . . . . .	48
The space in between . . . . .	48
The Power Amplifier . . . . .	49
The driver stage . . . . .	50
To NFB or not to NFB – that’s the question . . . . .	50
Building Octopus . . . . .	50
An MS Speaker System . . . . .	51
Speaker Connectivity . . . . .	51
PCB Bill of Materials . . . . .	52
<b>3. SBS: Side by Side dual beam tetrode SE power amplifier</b> . . . . .	<b>65</b>
The circuit . . . . .	65
Back to the circuit . . . . .	66
Bias settings . . . . .	66
Regulated screen grid and preamp/driver supply . . . . .	67
The Power Supply . . . . .	67
The Output Transformer . . . . .	67
Ultra Linear SE output transformers . . . . .	68
PCB versus tag board . . . . .	68
<b>4. Caviar – Nerd class-a in a bay</b> . . . . .	<b>71</b>
The Caviar amp . . . . .	71
The Power Supply . . . . .	72
Practical Design . . . . .	72
Assembly . . . . .	73

<b>5. Lightning – Extremist 2 x 24W triode class-A SE with 812A power triode . . . . .</b>	<b>81</b>
General . . . . .	81
Triode Technical Issues . . . . .	82
The Preamp . . . . .	82
Driver Stage . . . . .	83
Output Transformers . . . . .	84
The Power Supply . . . . .	84
Driver Stage Supply . . . . .	85
Preamp Tube Heater Supply . . . . .	85
Driver Heater Supply . . . . .	85
Power Tubes Heater Supply . . . . .	86
Bells and Whistles . . . . .	86
Performance . . . . .	87
Firing the Lightning up for the first time . . . . .	87
Printed Circuit Boards . . . . .	88
Epilogue . . . . .	89
Bill of Materials . . . . .	89
<b>6. Single Ended Channel amplifier with electronic cross-over . . . . .</b>	<b>101</b>
The Concept . . . . .	101
Treble Channel . . . . .	101
Bass Channel . . . . .	101
Preamp Tube . . . . .	102
Magic Eye . . . . .	102
The Power Supply . . . . .	102
The Speaker . . . . .	102
Visual Signal-to-Noise Ratio . . . . .	103
<b>7. WORKING MOJO – an approach to virtual damping factor . . . . .</b>	<b>105</b>
The Amp . . . . .	105
Damping Factor . . . . .	105
The POWRTRON and Stanley F. White . . . . .	106
The Circuit . . . . .	106
The MOJO Working . . . . .	108
The Driver Stage . . . . .	108
The Output Stage . . . . .	109
The Power Supply . . . . .	109
Working the MOJO . . . . .	110
The acid test goes like this: . . . . .	110
The Tag Board . . . . .	111
Printed Circuit Board . . . . .	112
Bills of Material (BOM) . . . . .	113
<b>8. A modular preamplifier . . . . .</b>	<b>125</b>
An Overview . . . . .	125
Channel Amplification versus bi-amping . . . . .	125
The main module . . . . .	126
<b>Electronic Crossover</b> . . . . .	127
The phono preamps . . . . .	128
Regulated power Supply . . . . .	129
Performance and considerations . . . . .	130
Bills of Material . . . . .	131
<b>9. Sterling Mixed mode/extended class-A 50W amplifier . . . . .</b>	<b>147</b>
The Circuit . . . . .	148
It’s Miller time! . . . . .	149
The Phase Splitter . . . . .	149

The preamp Stage . . . . .	149
Power Supply and Negative Bias . . . . .	150
The Screen Grid Voltage Regulator . . . . .	151
Bias adjustments . . . . .	151
Indicator Tube . . . . .	151
Building the Amp . . . . .	152
Measured Data . . . . .	152
<b>10. Saturday Night Special output transformerless 2 x 25W power amplifier . . . . .</b>	<b>157</b>
The Circuit . . . . .	157
Power Supply . . . . .	158
The Power Stage . . . . .	158
The Phase Splitter/driver . . . . .	159
First Amplification Stage . . . . .	159
Adjustment and connecting a transformer . . . . .	160
Matching Transformers . . . . .	161
Building It . . . . .	161
Heater Wiring . . . . .	162
Grounding . . . . .	162
<b>11. Play Your Willie: The Williamson Amplifier – with a twist . . . . .</b>	<b>165</b>
Is The Willy really a good amplifier then? . . . . .	165
The Original Williamson Design . . . . .	166
Was Williamson Wrong? . . . . .	166
Was Williamson wrong then? . . . . .	167
The Willie . . . . .	168
The Voltage Amplifier . . . . .	169
Alternative Driver Stages . . . . .	170
The Output Stage . . . . .	171
The CCS Explained . . . . .	171
The Output Transformer . . . . .	172
Switching Between Modes . . . . .	173
Switching On . . . . .	173
The Power Supply . . . . .	173
Summary . . . . .	174
Printed Circuit Driver Board . . . . .	174
Cathode feedback . . . . .	174
Adjustments . . . . .	175
Bills of Material (BOM) . . . . .	175
<b>12. HEADSUP Expensive Headphone Amplifier . . . . .</b>	<b>187</b>
Crossfeed . . . . .	187
The Main Circuit . . . . .	189
The Driver Circuit . . . . .	189
The Crossfeed Circuit . . . . .	190
The Power Supply . . . . .	191
Building Headsup . . . . .	191
The connector board . . . . .	192
Playing it . . . . .	192
Bills of Material (BOM) . . . . .	192
<b>13. RIAA and phono preamp stages . . . . .</b>	<b>203</b>
Phono preamps – a variation on a theme. . . . .	203
A little bit of history . . . . .	203
What is all this hue and cry about de-emphasis curves? . . . . .	203
The equalization curve . . . . .	205
The Designs . . . . .	205

RIAA using Pentode and triode SQ tubes . . . . .	205
Performance and considerations . . . . .	206
- and now for something completely different: The KYO . . . . .	207
A first glance . . . . .	207
The Circuit . . . . .	208
Input selector . . . . .	208
The amplifier stages . . . . .	208
De-emphasis circuits . . . . .	209
Power Supply . . . . .	209
VU Meters . . . . .	210
Performance and considerations . . . . .	210
OCTALS – a vintage tube RIAA preamp with shunt de-emphasis . . . . .	211
The Circuit . . . . .	211
Considerations . . . . .	212
Bills of Material (BOM) . . . . .	212
<b>14. PURISTE – straight SRPP preamp with pentode passive-RIAA . . . . .</b>	<b>229</b>
General circuit description (components reference to left channel except where common). . . . .	229
Tape Output . . . . .	229
The Line Amplifier Stage . . . . .	230
The Power Supply . . . . .	230
The Choke L3 . . . . .	231
Heatsink . . . . .	232
Capacitors in the power supply . . . . .	232
High Voltage and supply . . . . .	232
Practical build . . . . .	232
Bills of Material (BOM) . . . . .	233
<b>15. Q22: A QUAD 22 preamplifier clone . . . . .</b>	<b>237</b>
The Issues . . . . .	238
The Circuit in General . . . . .	239
Phono Preamp . . . . .	240
Plug-In Adapters . . . . .	240
Switching Circuits . . . . .	241
DISC Mode . . . . .	242
Volume Control . . . . .	242
Tape Output . . . . .	242
Line Amplification stage, Tone Controls and Low-pass Filter . . . . .	243
Tone Controls . . . . .	243
Low-pass Filter . . . . .	243
Power Amplifier Connection . . . . .	243
General Specifications . . . . .	244
Switching Logic . . . . .	245
Switch 1 and switch 10 . . . . .	245
20-pole header J <sub>1</sub> . . . . .	245
The Power Supply . . . . .	246
Bills of Material (BOM) . . . . .	247
<b>16. STRAIGHT – a simple ultra low noise preamplifier . . . . .</b>	<b>263</b>
The Circuit . . . . .	263
The Tone Control . . . . .	264
The Phono Amp Stage . . . . .	264
The Power Supply . . . . .	265
Setting Up . . . . .	266
Practical Experience . . . . .	266
Building The Straight . . . . .	267
Cooling Fins . . . . .	268

Input Switch . . . . .	268
Performance . . . . .	268
Bill of Materials . . . . .	269
<b>17. UNIDRIVE – a universal power tube driver with options . . . . .</b>	<b>277</b>
The UNIDRIVES . . . . .	277
UNIDRIVE I . . . . .	277
Heater Circuit . . . . .	277
Printed Circuit Board . . . . .	278
120W Amplifier . . . . .	278
Adjustments . . . . .	278
UNIDRIVE II . . . . .	279
UNIDRIVE II 30W Ultralinear Amplifier . . . . .	279
Stereo operation . . . . .	280
Bill of Materials . . . . .	280
<b>18. SUBSTORY – ultralinear PP 50W subwoofer amplifier with bass boost circuit . . . . .</b>	<b>287</b>
The circuit . . . . .	287
The Driver Stage . . . . .	287
Phase Splitter . . . . .	288
Preamp . . . . .	288
Bass Booster . . . . .	288
Power Supply . . . . .	289
Negative Bias Supply . . . . .	289
Layout . . . . .	289
<b>19. 3-way active crossover using miniature tubes . . . . .</b>	<b>291</b>
The circuit . . . . .	291
Schematics . . . . .	291
Building it . . . . .	292
Adjustments . . . . .	292
Bill of Materials . . . . .	293
<b>20. Variable active electronic crossover . . . . .</b>	<b>299</b>
<b>21. LIBRA balanced preamplifier . . . . .</b>	<b>301</b>
What is a balanced amplifier... . . . .	301
Application for a phono cartridge . . . . .	301
Amplifier noise . . . . .	302
The Circuit . . . . .	302
Mods for your turntable . . . . .	302
The Attenuator . . . . .	304
Conversion circuits . . . . .	304
Now for the output stages – a true challenge . . . . .	304
The Power Supply . . . . .	305
Performance . . . . .	305
<b>22. A balanced power amplifier . . . . .</b>	<b>313</b>
The input stage . . . . .	313
<b>23. The Volatile ultimate physiological volume control . . . . .</b>	<b>315</b>
Where are we going with all this? . . . . .	315
Correct Setup . . . . .	317
<b>24. The Leak Tweak – case for beefing up a TL12+ . . . . .</b>	<b>321</b>
A virtual rectifier tube . . . . .	322
More mods . . . . .	323
Constant Current Cathode Contraction . . . . .	323

Does it make a difference? . . . . .	324
Bill of Materials . . . . .	325
<b>25. Leak Stereo-60 Clone 2 x 30W ultra linear amplifier . . . . .</b>	<b>.335</b>
The Power Supply . . . . .	335
The Amplifier . . . . .	336
The Layout . . . . .	337
<b>26. Leak Point One preamplifier clone . . . . .</b>	<b>.339</b>
Back to Point One . . . . .	339
Is it worth building? . . . . .	339
<b>27. Microphone studio preamp with input attenuator . . . . .</b>	<b>.343</b>
The Power Supply . . . . .	343
Performance and considerations . . . . .	344
Construction . . . . .	344
Bills of Material (BOM) . . . . .	345
<b>28. The Tube – a stereo condenser microphone . . . . .</b>	<b>.349</b>
Back to business . . . . .	350
Output Capacitor and Transformer . . . . .	351
The Power Supply . . . . .	352
A Printed Circuit Board . . . . .	352
Performance . . . . .	352
<b>29. Conversion of Electret Microphones to Phantom-feed . . . . .</b>	<b>.357</b>
About Electret . . . . .	357
Electret Microphones . . . . .	357
Building it . . . . .	359
Performance . . . . .	359
Converting a small asymmetrical electret mike to phantom feed . . . . .	359
<b>30. M/S stereo recording techniques . . . . .</b>	<b>.363</b>
How to do M/S recordings . . . . .	363
What is actually happening here? . . . . .	363
Practical Considerations . . . . .	364
M – the center microphone versus the S-mike . . . . .	365
Recording . . . . .	365
<b>31. M/S to A-B decoder . . . . .</b>	<b>.367</b>
Now for the smart part . . . . .	367
Power Supply . . . . .	368
Printed Circuit board . . . . .	368
Bill of Materials . . . . .	368
<b>32. Line Level Stereo Compressor . . . . .</b>	<b>.373</b>
What does a compressor do? . . . . .	373
Types of Compressors . . . . .	374
6HZ6 . . . . .	375
The Power Supply . . . . .	376
Application . . . . .	376
Printed Circuit board . . . . .	376
Bill of Materials . . . . .	376
<b>33. Power supply for 8 vintage Neumann Microphones . . . . .</b>	<b>.383</b>
Practical Aspects . . . . .	385
<b>34. Power supply for a single Neumann vintage microphone . . . . .</b>	<b>.387</b>

<b>35. The Shrimp – Personal Guitar Amplifier Illustrations:</b> . . . . .	<b>389</b>
Amplifier Schematics . . . . .	389
The Reverb Unit . . . . .	390
Power Amplifier . . . . .	390
Power Supply . . . . .	391
Building The Shrimp . . . . .	391
Bill of Materials . . . . .	392
<b>36. The Mellow Yellow Studio Guitar Amplifier</b> . . . . .	<b>399</b>
The Mellow Yellow Knob . . . . .	399
The Dual Gain Controls. . . . .	400
The Reverb Circuit. . . . .	400
The Tremolo circuit . . . . .	400
Power Amp . . . . .	400
The Power Supply . . . . .	401
Adjustments . . . . .	401
Choice of speaker . . . . .	401
Box. . . . .	402
<b>37. The Gyratizer - 10-band parametric equalizer</b> . . . . .	<b>405</b>
What is a Gyrator? . . . . .	405
The Circuit . . . . .	405
Power Supply . . . . .	406
Performance . . . . .	406
Building The GYRATIZER . . . . .	406
<b>38. Continuo II – a compact 400W hybrid combo for upright bass</b> . . . . .	<b>409</b>
Background . . . . .	409
The Bass Booster . . . . .	411
The Mid Boost . . . . .	411
The Compressor . . . . .	411
The Equalizer . . . . .	412
The Output Stage . . . . .	413
Slide Potentiometers . . . . .	413
The Power Regulator . . . . .	413
The Speaker and Enclosure . . . . .	414
Printed Circuit board . . . . .	415
Adjustments . . . . .	415
Hooking up to a power amplifier . . . . .	415
Line Output . . . . .	416
Bill of Materials . . . . .	416
<b>39. Capacitor Test Jig Illustrations</b> . . . . .	<b>425</b>
<b>40. Roadies Disgust – 300W RMS all tube bass amplifier.</b> . . . . .	<b>427</b>
The Circuit . . . . .	427
The power Amplifier. . . . .	428
Line outputs . . . . .	429
The power Supply . . . . .	429
The Preamplifier . . . . .	430
Equalizer . . . . .	430
Performance . . . . .	431
<b>Index</b> . . . . .	<b>435</b>